

# Circuits and Transforms

Aditya Gangula EP20BTECH11001\*

## CONTENTS

**Abstract—**This manual provides a simple introduction to Transforms

## 1 DEFINITIONS

1. The unit step function is

$$u(t) = \begin{cases} 1 & t > 0 \\ \frac{1}{2} & t = 0 \\ 0 & t < 0 \end{cases} \quad (1.1)$$

2. The Laplace transform of  $g(t)$  is defined as

$$G(s) = \int_{-\infty}^{\infty} g(t)e^{-st} dt \quad (1.2)$$

## 2 LAPLACE TRANSFORM

1. In the circuit, the switch S is connected to position P for a long time so that the charge on the capacitor becomes  $q_1 \mu C$ . Then S is switched to position Q. After a long time, the charge on the capacitor is  $q_2 \mu C$ .

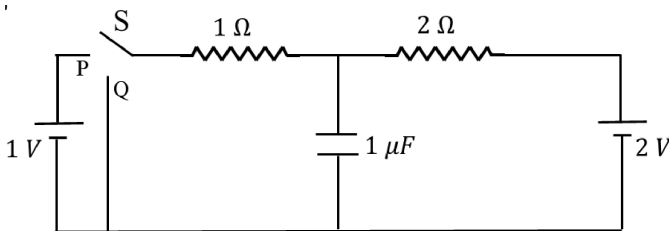


Fig. 2.1


2. Draw the circuit using latex-tikz.

**Solution:**

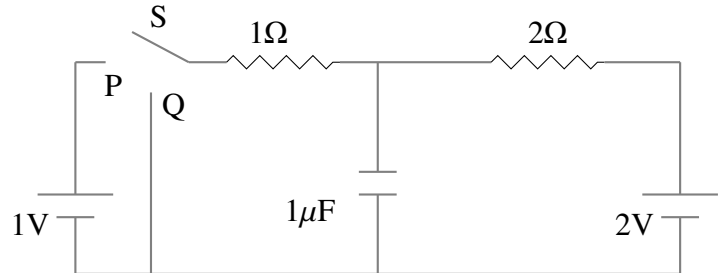3. Find  $q_1$ .

**Solution:** No current will pass through the capacitor, hence

$$i = \frac{2 - 1}{2 + 1} = \frac{1}{3} A$$



$$V_c = 2 - 2i = \frac{4}{3} V$$

$$q_1 = \frac{4}{3} \mu C$$

4. Show that the Laplace transform of  $u(t)$  is  $\frac{1}{s}$  and find the ROC.

**Solution:**

$$\begin{aligned} U(s) &= \int_{-\infty}^{\infty} u(t)e^{-st} dt \\ &= \int_0^{\infty} e^{-st} dt = \frac{1}{s}, \quad s > 0 \end{aligned}$$

5. Show that

$$e^{-at}u(t) \xleftrightarrow{\mathcal{H}} L \frac{1}{s+a}, \quad a > 0 \quad (2.1)$$

and find the ROC.

**Solution:**

$$\begin{aligned} &= \int_{-\infty}^{\infty} u(t)e^{-at}e^{-st} dt \\ &= \int_0^{\infty} e^{-(s+a)t} dt \\ &= \frac{1}{s+a}, \quad s+a > 0 \end{aligned}$$

6. Now consider the following resistive circuit transformed from Fig. ?? where

$$u(t) \xleftrightarrow{\mathcal{H}} LV_1(s) \quad (2.2)$$

$$2u(t) \xleftrightarrow{\mathcal{H}} LV_2(s) \quad (2.3)$$

Find the voltage across the capacitor  $V_{C_0}(s)$ .

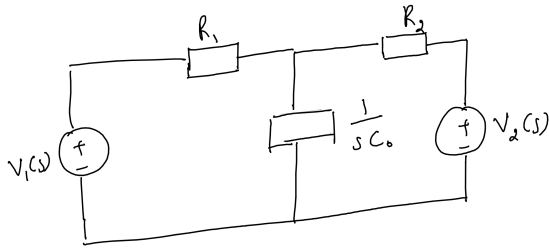


Fig. 2.2

**Solution:** From Q2.4

$$V_1(s) = \frac{1}{s} \quad V_2(s) = \frac{2}{s}$$

$$\frac{V_1 - V_C}{R_1} + \frac{V_2 - V_C}{R_2} - V_C sC = 0$$

simplifying,

$$\Rightarrow V_C(s) = \frac{2R_1 + R_2}{R_1 + R_2} \left( \frac{1}{s} - \frac{1}{\frac{R_1 + R_2}{R_1 R_2 C} + s} \right)$$

7. Find  $v_{C0}(t)$ . Plot using python.

**Solution:** Using the inverse Laplace transform from the obtained  $V_C(s)$  we get,

$$v_C(t) = \frac{2R_1 + R_2}{R_1 + R_2} u(t) \left( 1 - e^{-\frac{R_1 + R_2}{R_1 R_2 C} t} \right)$$

$$R_1 = 1\Omega \quad R_2 = 2\Omega \quad C = 1\mu F$$

$$v_C(t) = \frac{4}{3} u(t) \left( 1 - e^{-1.5 \times 10^6 t} \right)$$

wget <https://github.com/Galahad7377/EE3900/blob/main/cktsig/codes/2.7.py>

8. Verify your result using ngspice.

**Solution:**

wget <https://github.com/Galahad7377/EE3900/blob/main/cktsig/codes/2.8.cir>

9. Obtain Fig. ?? using the equivalent differential equation.

**Solution:**

$$\frac{dq}{dt} = \frac{V_1 - V_C}{R_1} + \frac{V_2 - V_C}{R_2}$$

$$\frac{dq}{dt} = 1 - \frac{q}{C} + \frac{1}{2} \left( 2 - \frac{q}{C} \right)$$

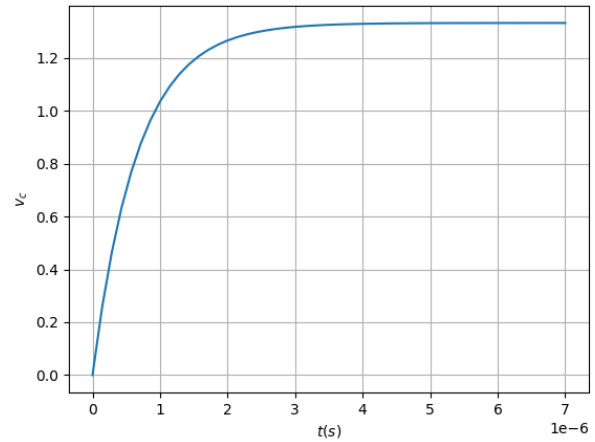
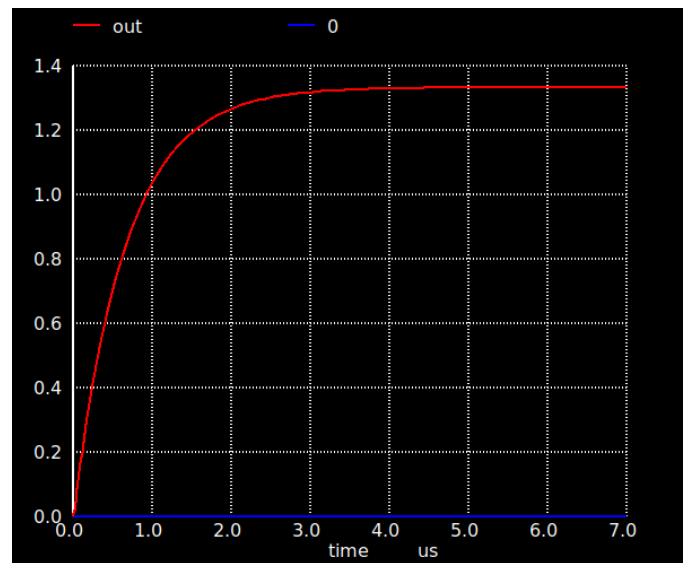
Fig. 2.3:  $v_C(t)$ 

Fig. 2.4

simplifying and integrating,

$$\int_0^{q_1} \frac{dq}{2 - 1.5q/C} = \int_0^t dt$$

$$\ln \frac{2 - 1.5q/C}{2} = 1.5 \frac{t}{C}$$

$$\Rightarrow q_1 = \frac{4}{3} \left( 1 - e^{-1.5 \times 10^6 t} \right) \times 10^{-6}$$

### 3 INITIAL CONDITIONS

1. Find  $q_2$  in Fig. ??.

**Solution:**

$$i = \frac{2}{1+2} = \frac{2}{3} A$$

$$V_c = 2 - 2.i = \frac{2}{3}V$$

$$\Rightarrow q_2 = CV_c = \frac{2}{3}\mu C$$

2. Draw the equivalent  $s$ -domain resistive circuit when S is switched to position Q. Use variables  $R_1, R_2, C_0$  for the passive elements. Use latex-tikz.

**Solution:**

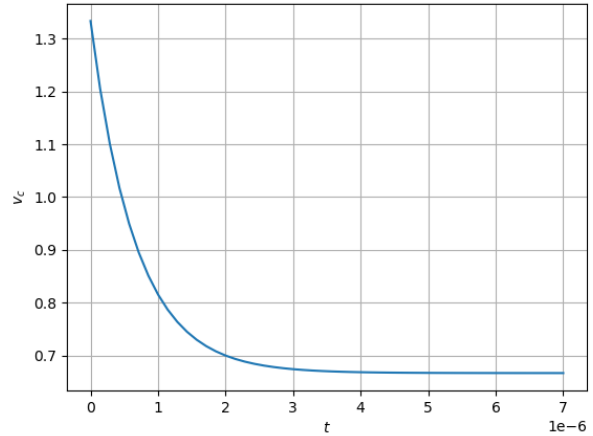
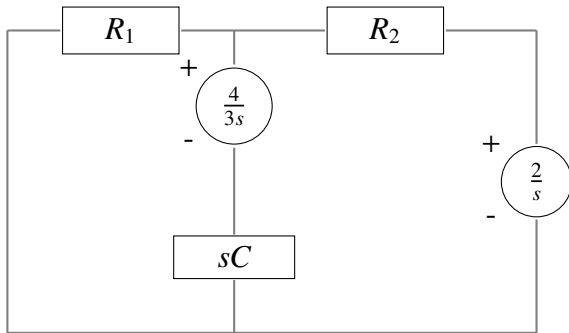


Fig. 3.1:  $v_c(t)$

3.  $V_{C_0}(s) = ?$

**Solution:**

$$\frac{V_C - 2/s}{R_2} + \frac{V_C}{R_1} + (V_C - 4/3s)sC = 0$$

$$V_C(s) = \frac{\frac{2}{sR_2} + \frac{4}{3}C}{\frac{1}{R_1} + \frac{2}{R_2} + sC}$$

4.  $v_{C_0}(t) = ?$  Plot using python.

**Solution:** Further simplifying,

$$V_C(s) = \frac{4}{3} \left( \frac{1}{\frac{R_1+R_2}{R_1R_2C} + s} \right) + \frac{2R_1R_2}{R_2(R_1+R_2)} \left( \frac{1}{s} - \frac{1}{\frac{R_1+R_2}{R_1R_2C} + s} \right)$$

Using the inverse Laplace transform from the obtained  $V_C(s)$  we get,

$$v_c(t) = \frac{4}{3} e^{\frac{R_1+R_2}{R_1R_2C} t} + \frac{2R_1R_2}{R_2(R_1+R_2)} \left( 1 - e^{\frac{R_1+R_2}{R_1R_2C} t} \right)$$

$$R_1 = 1\Omega \quad R_2 = 2\Omega \quad C = 1\mu F$$

$$\Rightarrow v_c(t) = \frac{2}{3} u(t) (1 + e^{-1.5 \times 10^6 t})$$

wget <https://github.com/Galahad7377/EE3900/blob/main/cktsig/codes/3.4.py>

5. Verify your result using ngspice.

**Solution:**

wget <https://github.com/Galahad7377/EE3900/blob/main/cktsig/codes/3.5.cir>

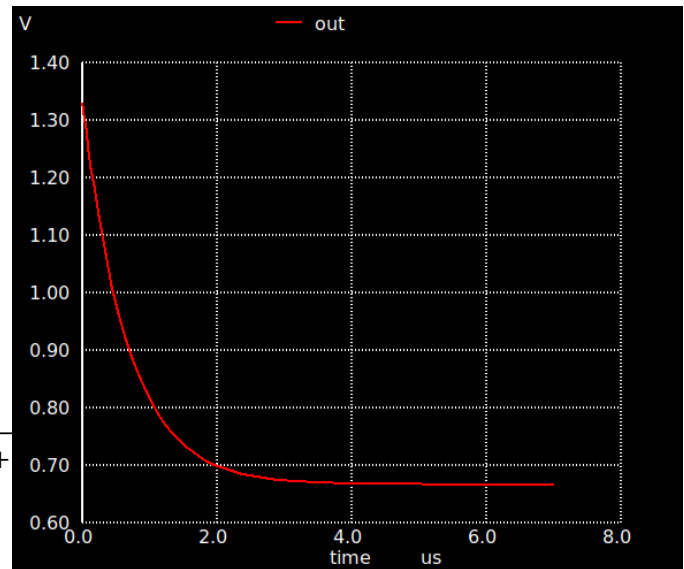


Fig. 3.2

6. Find  $v_{C_0}(0-)$ ,  $v_{C_0}(0+)$  and  $v_{C_0}(\infty)$ .

**Solution:** from section 2,

$$v_c(0-) = \frac{4}{3}V$$

from Q3.4

$$v_c(0+) = \frac{4}{3}V$$

$$v_c(\infty) = \frac{2}{3}V$$

7. Obtain the Fig. in problem ?? using the equivalent differential equation.

**Solution:**

$$\frac{dq}{dt} = \frac{2 - V_C}{2} - V_C$$

simplifying and integrating,

$$\int_{4/3\mu C}^q \frac{dq}{2 - 3q/C} = 2 \int_0^t dt$$

$$\ln \frac{2 - 3q/C}{-2} = -1.5 \frac{t}{C}$$

$$q = \frac{2}{3} \left( 1 + e^{-1.5 \times 10^6 t} \right) \times 10^{-6}$$

#### 4 BILINEAR TRANSFORM

1. In Fig. ??, consider the case when  $S$  is switched to  $Q$  right in the beginning. Formulate the differential equation.
2. Find  $H(s)$  considering the output voltage at the capacitor.
3. Plot  $H(s)$ . What kind of filter is it?
4. Using trapezoidal rule for integration, formulate the difference equation by considering

$$y(n) = y(t)|_{t=n} \quad (4.1)$$

5. Find  $H(z)$ .
6. How can you obtain  $H(z)$  from  $H(s)$ ?